
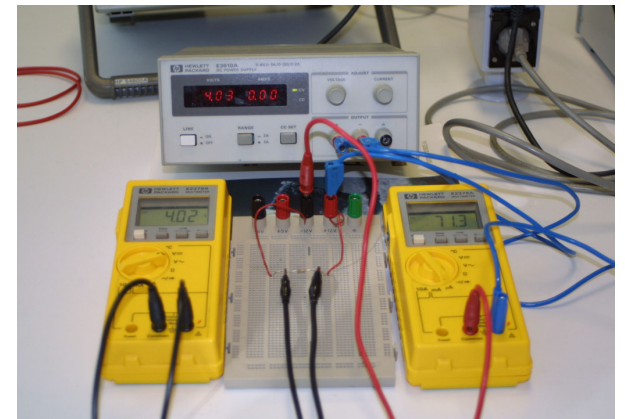


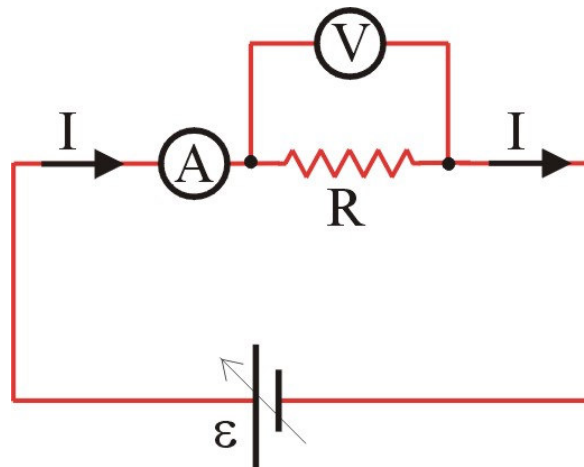

Experiment # 1: DC Measurements

- **Multimeter:**
 - Measurements of DC voltage and current, and resistance
 - Errors introduced by the multimeter
- **Ohm's Law for Direct Current:**
 - experiment: 'short' and 'long' arrangement
- **Maximum Power Transfer Theorem**





303 – Physics for Engineers II - Laboratory

Multimeter (1/2)



Used as an ohmmeter (it measures Ω),
voltmeter (V), ammeter (I)

-Ammeter: current measurement
(in series)



-Voltmeter: voltage measurement
(in parallel)



-Ohmmeter: resistance measurement
resistor must be isolated from the rest of the circuit


Please, pay attention to input terminals (“jacks”) and to the range selected!!!

Multimeter (2/2)

Errors when using a multimeter:


- uncertainty of the device: digitising error and precision
- perturbations introduced in the circuit by the instrument

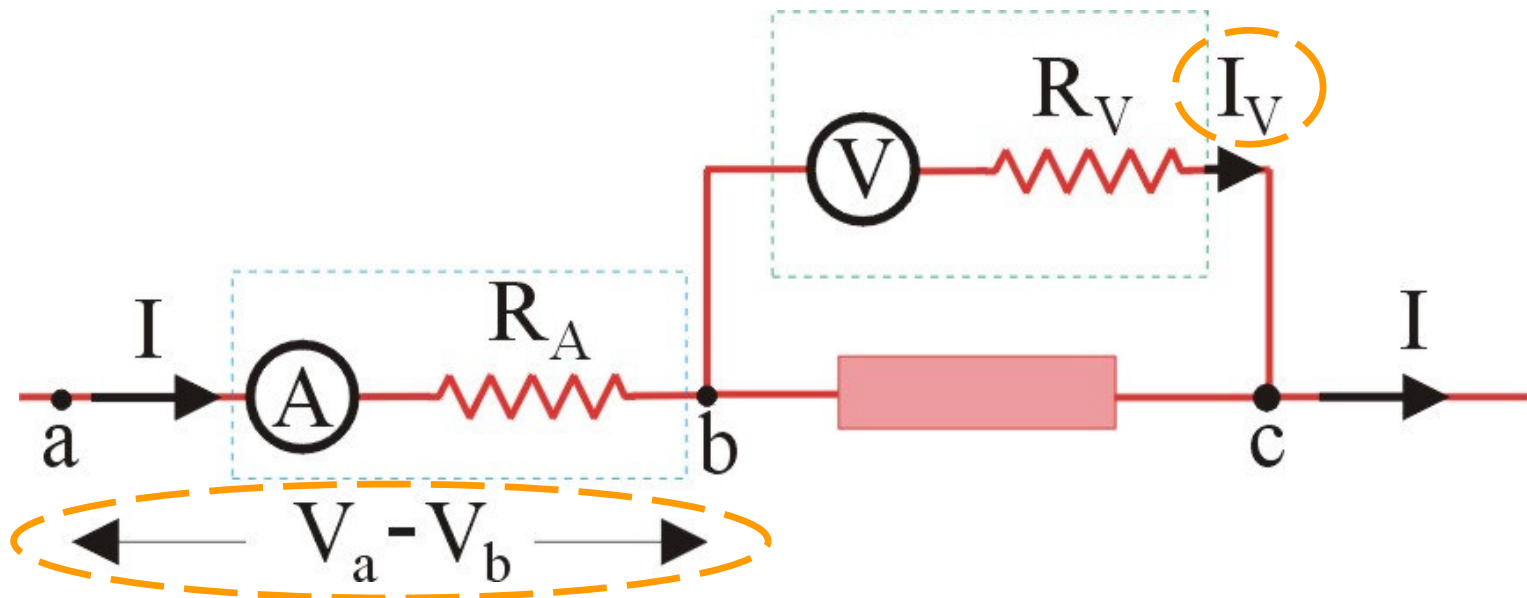Ideal ($R_V = \infty$, $R_A = 0$) and **real** multimeters:







Ohm's Law

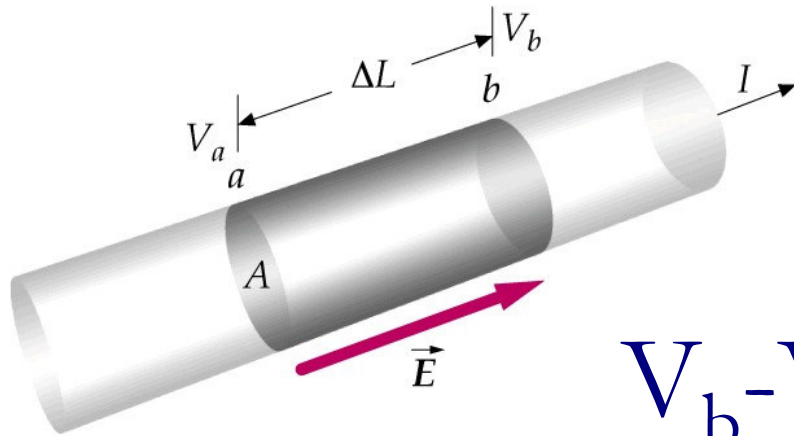

$$V_b - V_a = I \cdot R$$

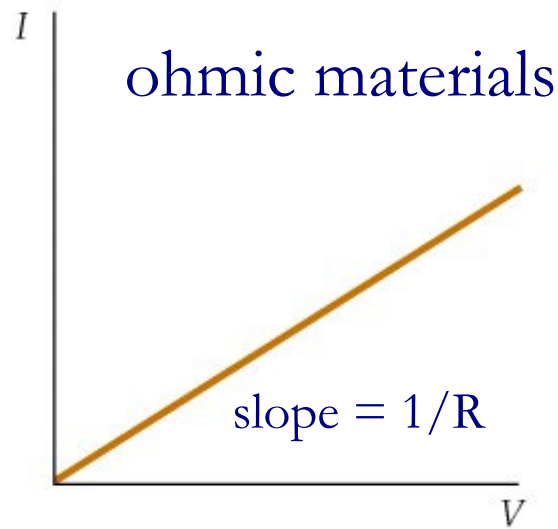

(a)

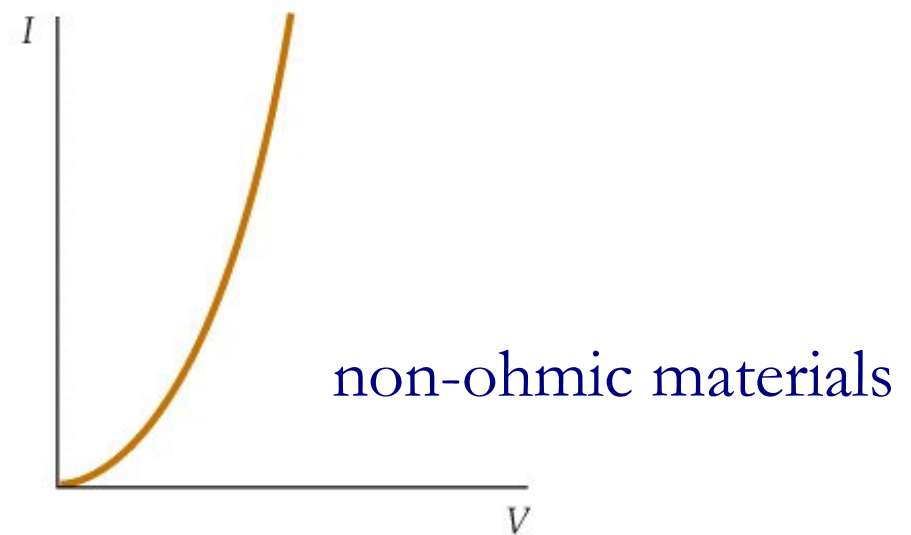


(b)




Resistance measurement from

Ohm's Law

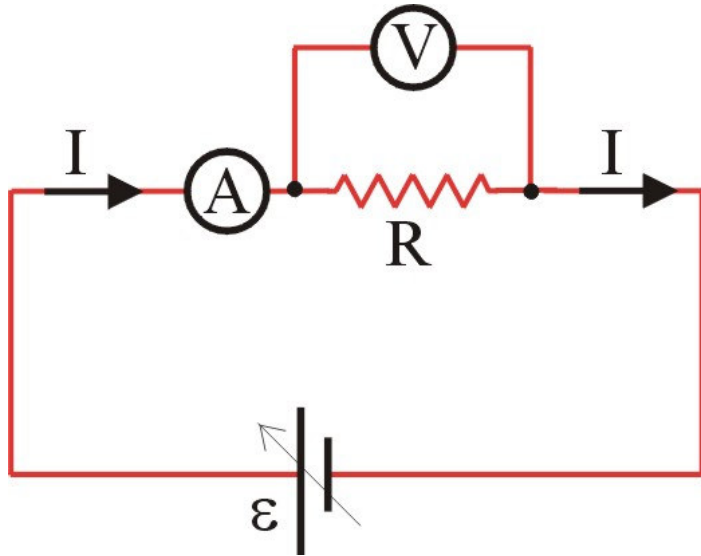

“Short” arrangement:
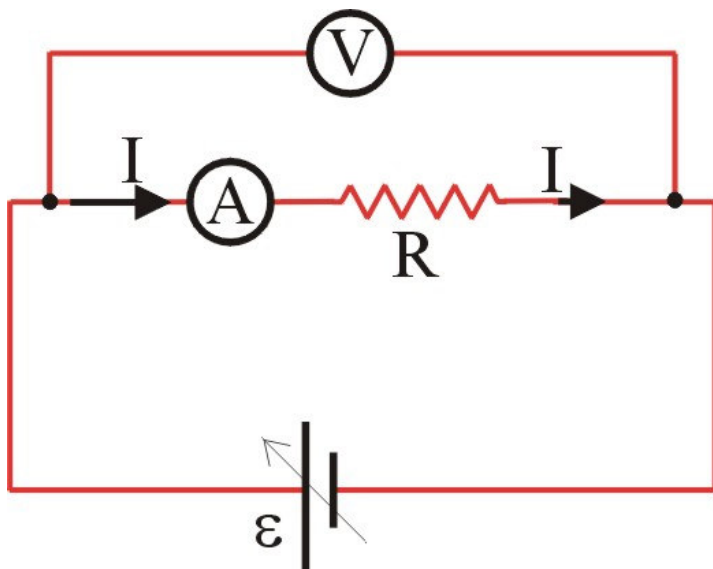
$$\frac{1}{R_{short}} = \frac{1}{R} + \frac{1}{R_V}$$



“Long” arrangement:

$$R_{long} = R + R_A$$

$$V = I \cdot R$$

Same value for R only if $R_V = \infty$, $R_A = 0$ ⁵



Maximum Power Transfer Theorem

(Jacobi's Theorem) (1/2)


Work done by the electrostatic field,
change in electrostatic potential energy:

$$W = q(V_b - V_c)$$

$$W = I(V_b - V_c)t$$

Following Ohm's Law: $W = I^2 R t$

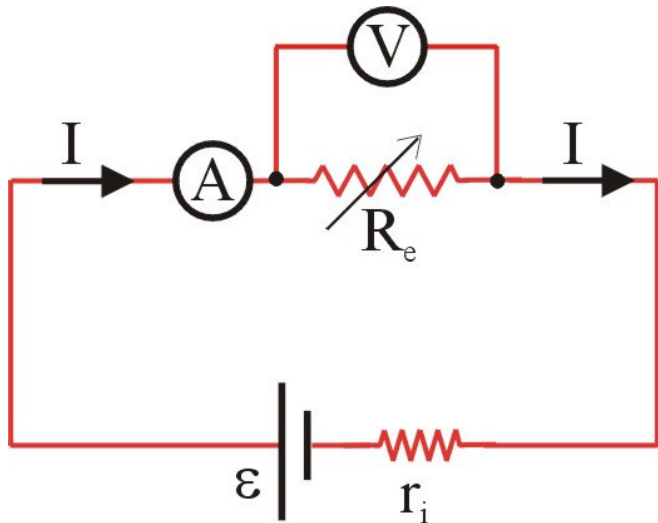Power dissipated in the load: $P = I^2 R = I(V_b - V_c)$




$$I = \frac{\varepsilon}{R_e + r_i}$$

Power
dissipated in R_e : $P_e = \frac{\varepsilon^2 R_e}{(r_i + R_e)^2} = V \cdot I$



Maximum Power Transfer Theorem

(Jacobi's Theorem) (2/2)

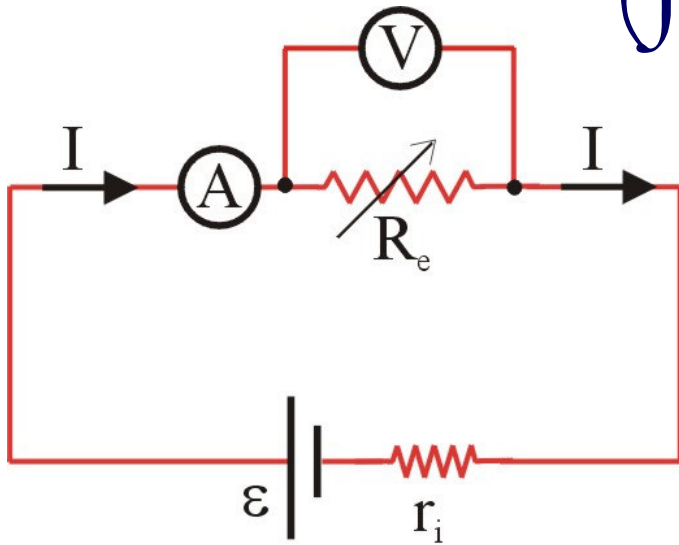

$$P_e = \frac{\varepsilon^2 R_e}{(r_i + R_e)^2} = V \cdot I \quad \frac{\partial P_e}{\partial R_e} = 0 \Rightarrow R_e = r_i$$

Maximum Power Transfer Theorem:

Maximum power is transferred when the internal resistance of the source equals the resistance of the load (when the external resistance can be varied and internal resistance is constant)

$$I = \frac{\varepsilon}{R_e + r_i} \implies R_e = \frac{\varepsilon}{I} - r_i$$

To obtain r_i : linear regression, R_e vs. $1/I$




Experimental procedure

1. Find the nominal value of a pair of resistors using colour codes
2. Measure their resistance with a multimeter and their association in series and in parallel
 - 3.1. “Short” arrangement for only one of the resistors (vary the voltage from 1 V to 10 V in steps of 1 V): table $\mathcal{E}(I)$, plot and least-squares fit, determination of R
 - 3.2. “Long” arrangement (same procedure)
4. Maximum power transfer theorem: emf = 1V, rheostat (variable resistor) $R_e = 2-9 \Omega$, steps of 1Ω , measure rheostat's resistance with ohmmeter (always disconnect power from resistor), plot and fit, determination r_i , plots of P_e , P_i , η .



303 – Physics for Engineers II - Laboratory

Resistors

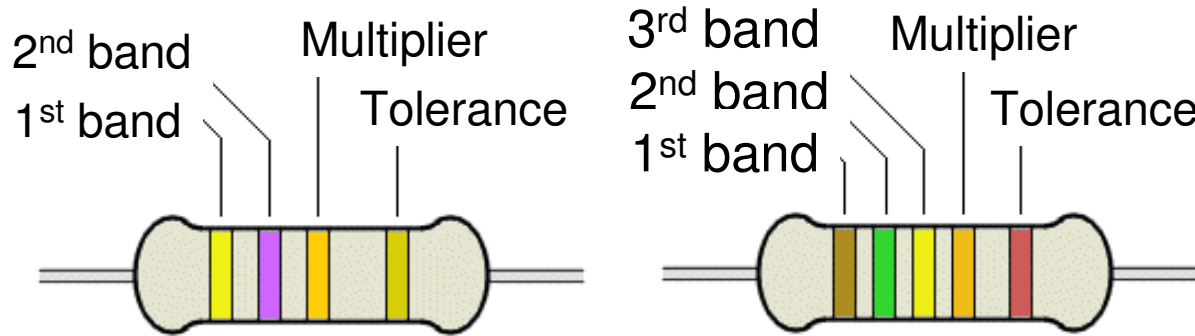


COLOUR	1 st band	2 nd band	3 rd band	Multiplier	Tolerance
Silver				x 0.01	10%
Gold				x 0.1	5%
Black	0	0	0	x 1	
Brown	1	1	1	x 10	1%
Red	2	2	2	x 100	2%
Orange	3	3	3	x 1000	
Yellow	4	4	4	x 10000	
Green	5	5	5	x 100000	0.5%
Blue	6	6	6	x 1000000	
Violet	7	7	7		
Grey	8	8	8		
White	9	9	9		
--None--	-	-	-		20%



How to read resistor colour codes

COLOUR	1 st band	2 nd band	3 rd band	Multiplier	Tolerance
Silver				x 0.01	10%
Gold				x 0.1	5%
Black	0	0	0	x 1	
Brown	1	1	1	x 10	1%
Red	2	2	2	x 100	2%
Orange	3	3	3	x 1000	
Yellow	4	4	4	x 10000	
Green	5	5	5	x 100000	0.5%
Blue	6	6	6	x 1000000	
Violet	7	7	7		
Grey	8	8	8		
White	9	9	9		
--None--	-	-	-		20%

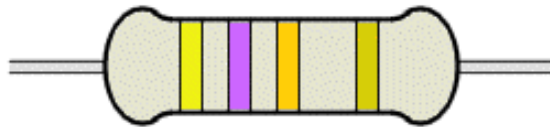

Left resistor:

yellow – violet – orange – gold

4 – 7 – 3 zeros, 5% tolerance

$47000 \Omega = 47 \text{ k}\Omega$

Real value between 44650Ω and 49350Ω

$(47 \text{ k}\Omega \pm 5\%)$



Right resistor (one more band)

precision resistor: tolerance 2%

brown – green – yellow – orange

1 – 5 – 4 – 3 zeros, 2% tolerance

$154000 \Omega = 154 \text{ k}\Omega = 0.154 \text{ M}\Omega$

Real value between $150.9 \text{ K}\Omega$ and $157.1 \text{ K}\Omega$

$(154 \text{ k}\Omega \pm 2\%)$.



Multimeter measurement accuracy

Uncertainty of the multimeter (digitising error and instrument precision):

$$\% \text{ measurement} + (\text{digits} \cdot \text{resolution})$$

Multimeter HP E2378A

Function	Range	Resolution	Accuracy ± (% rdg + number of digits)	
			E2373A	E2377A E2378A
dc voltage	300 mV	100 μV	0.5% + 2	0.3% + 2
	3 V	1 mV	0.5% + 1	0.3% + 2
	30 V	10 mV	0.5% + 1	0.4% + 1
	300 V	100 mV	0.7% + 1	0.4% + 1
ac voltage	1000 V	1 V	0.7% + 1	0.4% + 1
	3 V	1 mV	1.2% + 4	1.0% + 3
	30 V	10 mV	1.2% + 4	1.0% + 3
	300 V	100 mV	1.2% + 4	1.0% + 3
dc current	750 V	1 V	1.2% + 4	1.0% + 3
	300 μA	100 nA	—	1.0% + 2
	3 mA	1 μA	—	1.0% + 2
	30 mA	10 μA	1.0% + 2	1.0% + 2
ac current	300 mA	100 μA	1.5% + 2	1.5% + 2
	10 A	10 mA	1.5% + 2	1.5% + 2
	300 μA	100 nA	—	2.0% + 5
	3 mA	1 μA	—	2.0% + 5
Resistance	30 mA	10 μA	2.0% + 5	2.0% + 5
	300 mA	100 μA	2.0% + 5	2.0% + 5
	10 A	10 mA	2.0% + 5	2.0% + 5
	300 Ω	100 mΩ	0.7% + 2	0.7% + 2
	3 kΩ	1 Ω	0.7% + 1	0.7% + 1
	30 kΩ	10 Ω	0.7% + 1	0.7% + 1
	300 kΩ	100 Ω	0.7% + 1	0.7% + 1
	3 MΩ	1 kΩ	1.5% + 1	0.7% + 1
	300 MΩ	10 kΩ	3.0% + 1	2.0% + 1

Multimeter Promax PD751

Voltage

Range	Resolution	DC Accuracy	AC Accuracy*	Input Impedance	Max. Input
400.0 mV	0.1 mV	±(0.3% meas+5 dig)	±(1.5% meas+5dig)	100 MΩ	1000 V DC or AC peak <10 s
4.000 V	1 mV	±(0.1% meas+5 dig)	±(1.0% meas+5dig)	10 MΩ	
40.00 V	10 mV	PD-751 ±(0.5% meas+5 dig)	(40 – 1 kHz) PD-751 (40 – 500 Hz) PD-750		
400.0 V	100 mV	PD-750	±(1.5% meas+5dig)		
1000 V	1 V	±(0.5% meas.+5 dig)	(700V)		

Current

Range	Resolution	DC Accuracy	AC Accuracy*	Max. Input	Overload Protection
400.0 μA	0.1 μA	±(1.2% meas+10dig)	±(1.5% meas+10dig) (40 – 1 kHz) PD-751 (40 – 500 Hz) PD-750	400 mA	fuse 0,5 A/250 V
4000 μA	1 μA				
40.00 mA	10 μA				
400.0 mA	100 μA				
20.00 A	1 mA	±(2% meas+10dig)	±(2% meas+10dig)	20 A, < 30 s (every 15 min.)	fuse 20 A/250 V

Frequency

Range	Resolution	Accuracy	Max. Input
5.000 Hz	0.001 Hz	±(0.1% meas+2dig) (250 mVac peak minimum)	250 V DC or CA peak
50.00 Hz	0.01 Hz		
500.0 Hz	0.1 Hz		
5.000 kHz	1 Hz		
50.00 kHz	10 Hz		
500.0 kHz	100 Hz		
5.000 MHz	1 kHz		
10.00 MHz	10 kHz		

Resistance

Range	Resolution	Accuracy	Max. Input
400 Ω	0.1 Ω	± (0.5% meas + 10dig)	250V DC or AC peak
4.000 kΩ	1 Ω		
40.00 kΩ	10 Ω		
400.0 kΩ	100 Ω		
4000 kΩ	1 kΩ		
40 MΩ	10 kΩ	±(1% meas+5dig)	



Questions

1.- Discuss why equations (2) and (3) in the lab manual provide the resistances measured for the ‘short’ and ‘long’ arrangement.

Justify why $R_{\text{short}} < R < R_{\text{long}}$.

Estimate the internal resistances of the ammeter and the voltmeter.

2.- Compare your experimental results with the series and parallel combination rules for resistors.

3.- Show that the maximum of the function $P_e = P_e(R_e)$ is obtained when $R_e = r_i$.

4.- Describe qualitatively how P_i and η change when we vary R_e .

5.- Which value of R_e gives a performance of 0.5?. What happens with P_i and P_e for this value of R_e ?