



Experiment # 2:

Digital oscilloscope. RC Circuit


- **Introduction to oscilloscopes:** measuring transient and periodic signals. Digital oscilloscope
- **Condensers and capacitance**
- **Making measurements with the oscilloscope:** probe attenuation factor, automatic measurements, cursor measurements, main and delayed sweep, trigger, ambient signals, signals from function generator
- **Discharging a capacitor in an RC Circuit:** time constant
- **RC integrator and differentiator**



Periodic signals

Multimeter: measures V, I, R (only DC signals or low frequency, ~50 Hz / kHz)

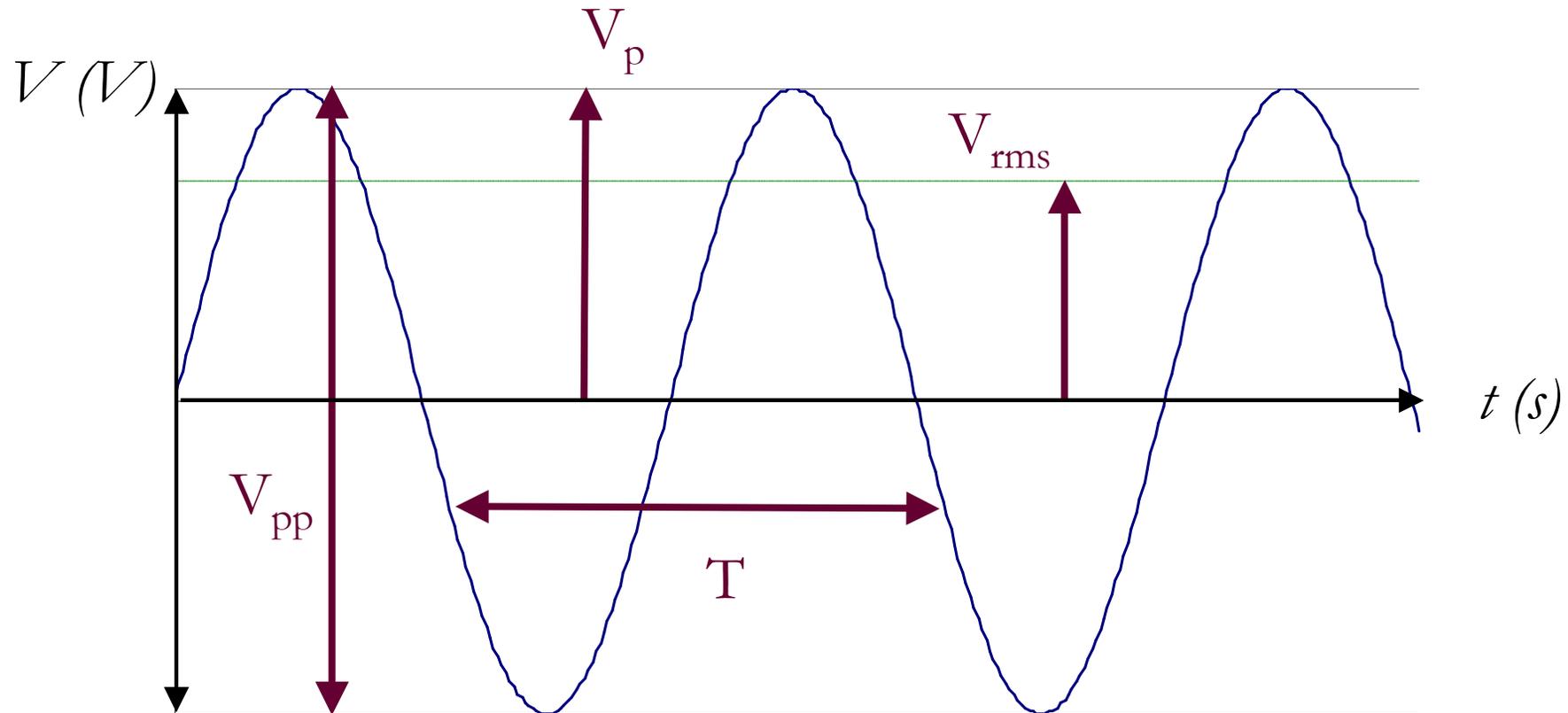Oscilloscope: signals $V(t)$, $V_1(t)$ vs. $V_2(t)$, up to very high frequency (60 MHz and more)



$$T = \frac{1}{\nu} = \frac{2\pi}{\omega}$$

$$V_{rms} = \sqrt{\text{avg}(V^2)}$$

$$\text{for a sinusoidal signal: } V_{rms} = \frac{V_p}{\sqrt{2}} = \frac{V_{pp}}{2\sqrt{2}}$$




UNIVERSITAT
JAUME I


303 – Physics for Engineers II - Laboratory

Digital oscilloscope

Analog oscilloscope

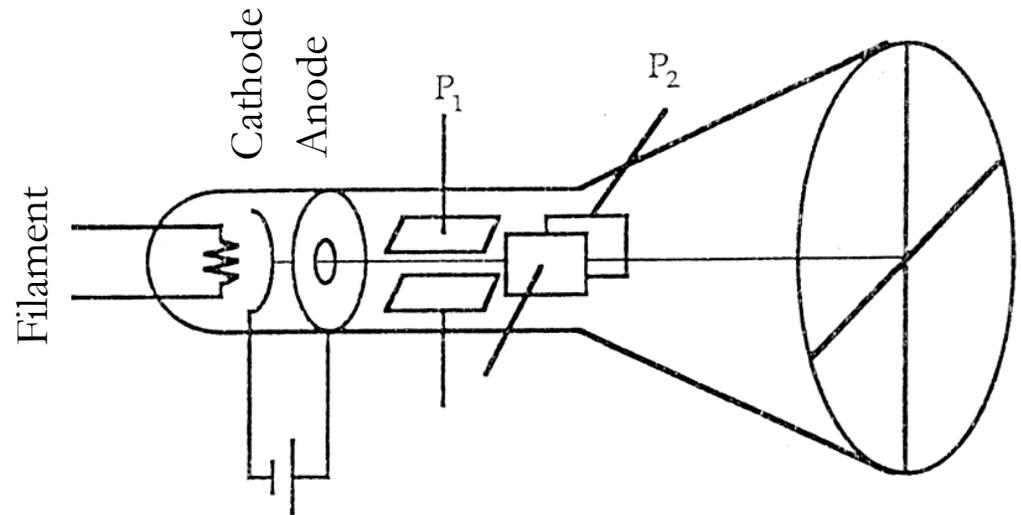


Digital
oscilloscope

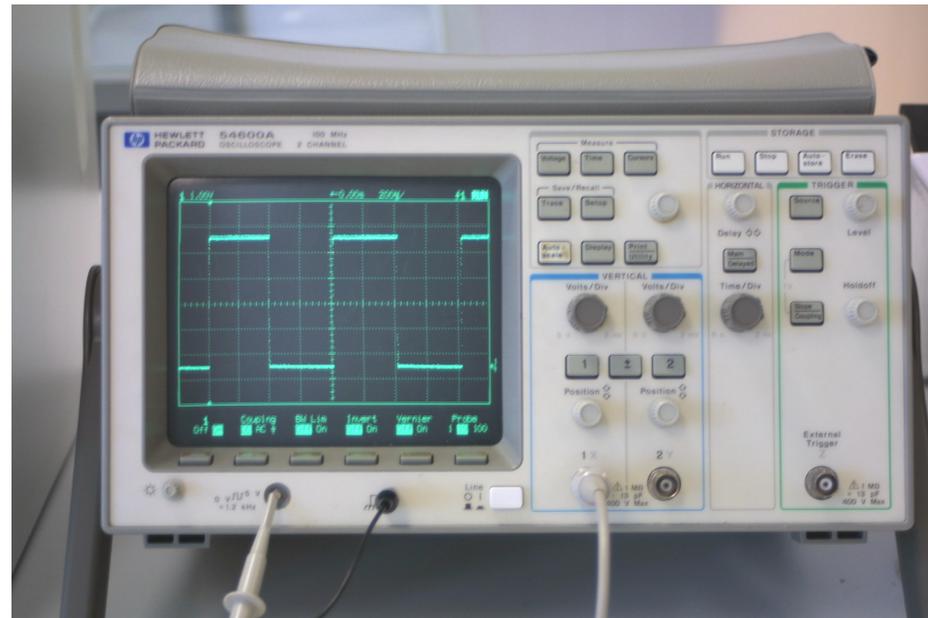





Scope trigger

Transient signal

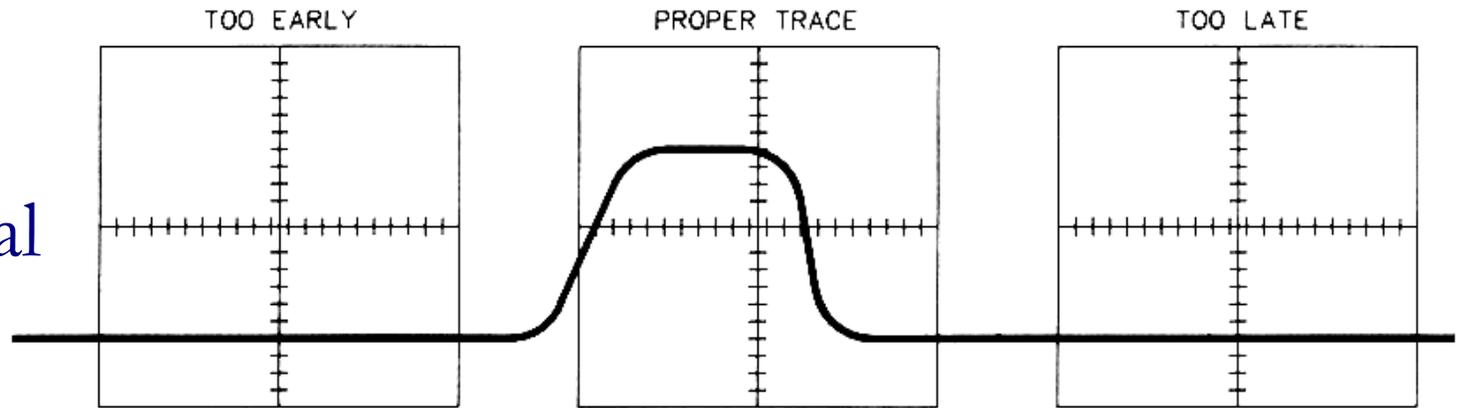


Periodic signal

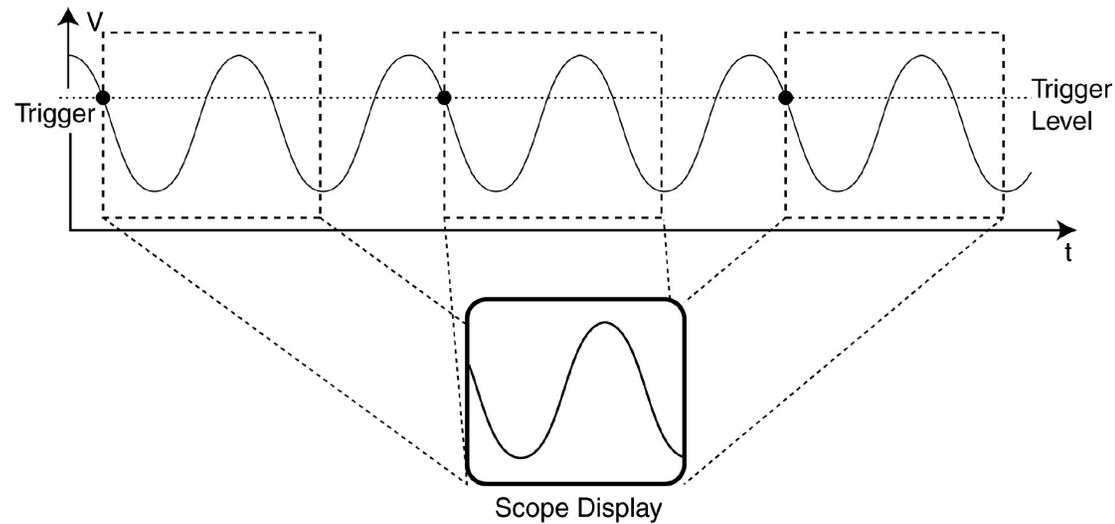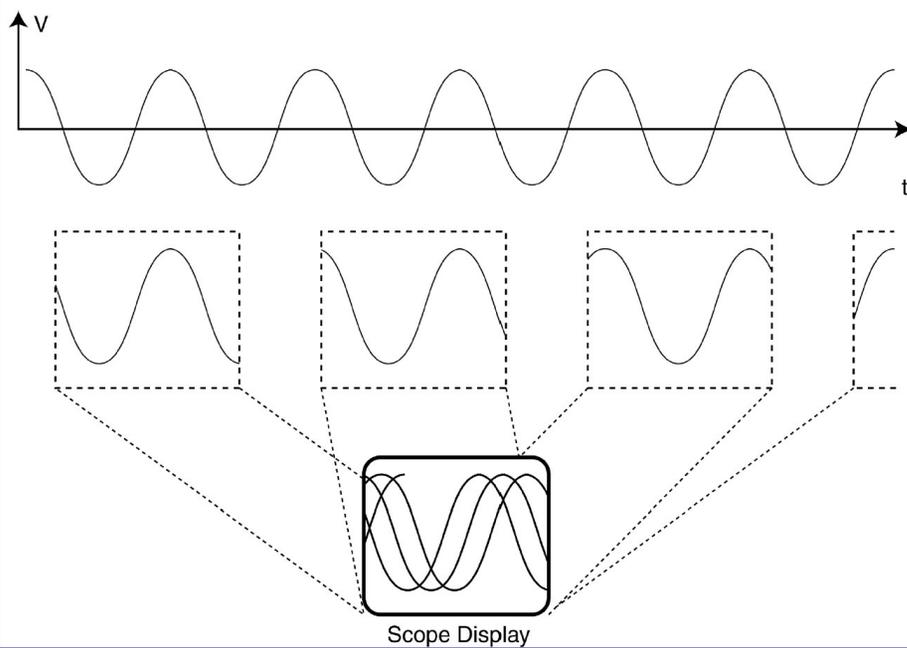




303 – Physics for Engineers II - Laboratory

Capacitors

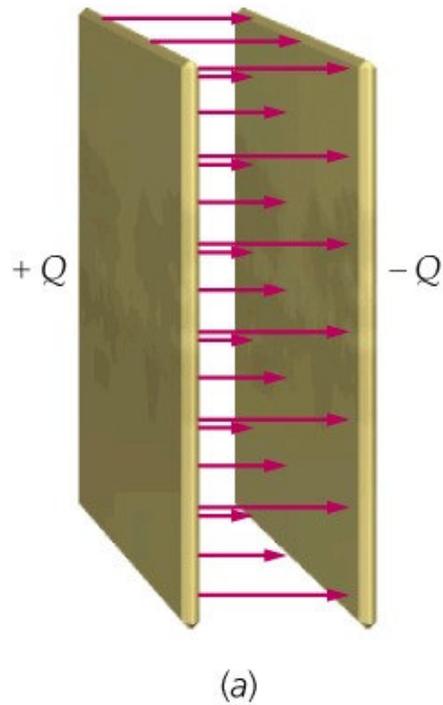

$$C = \frac{Q}{V}$$

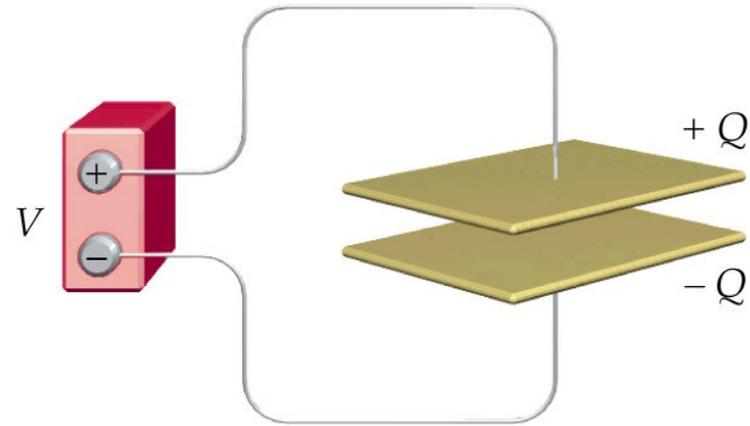


Applications:

Electronics, low-pass and high-pass filter


Keyboards: capacitance switch

Camera flash

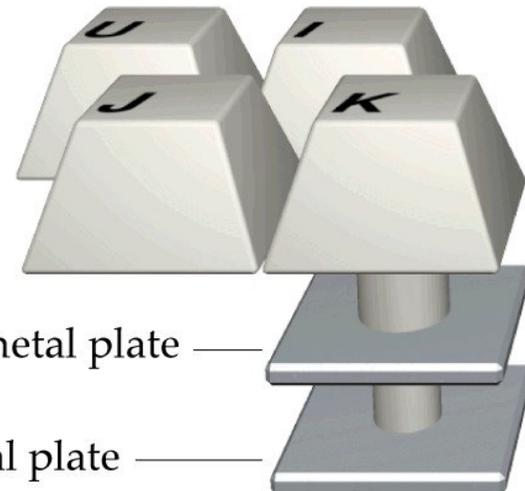



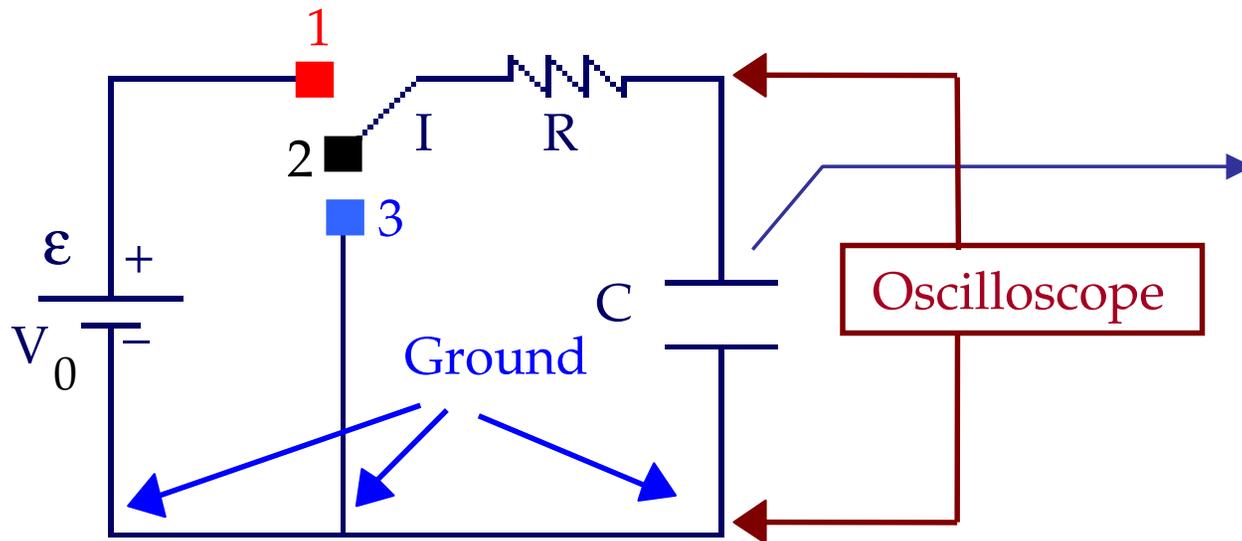RC Circuit: Discharging a capacitor (1/2)



$$dq = -i dt$$

$$V(t) = \frac{q(t)}{C} = i(t) R$$

$$\frac{dq}{q} = -\frac{1}{RC} dt$$

$$\frac{q(t)}{C} = -R \frac{dq}{dt}$$

$$\int_{Q_0}^Q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt$$



RC Circuit : Discharging a capacitor (2/2)

$$\int_{Q_0}^Q \frac{dq}{q} = -\frac{1}{RC} \int_0^t dt \quad Q(t) = Q_0 e^{-\frac{t}{RC}}$$

$$\tau = RC$$


$$V(t) = \frac{Q(t)}{C} = \frac{Q_0}{C} e^{-\frac{t}{RC}} = V_0 e^{-\frac{t}{RC}}$$

$$\ln V = -\frac{t}{RC} + \ln V_0$$

$$\text{pendent} = -\frac{1}{RC}$$



RC integrator

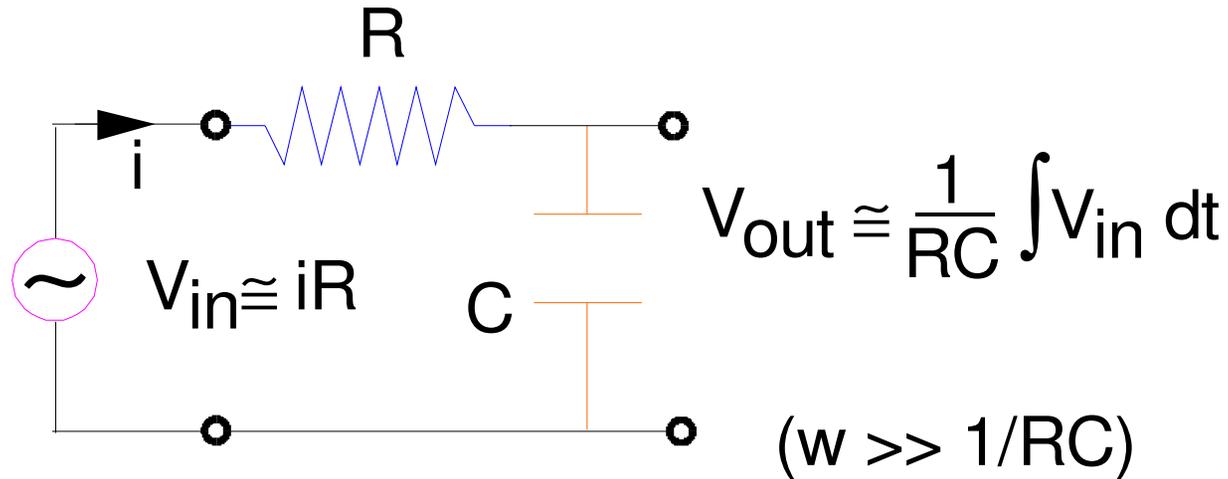

$$V_{in} = I \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$$


$$\omega C \gg R \Rightarrow V_{in} \cong IR$$

$$V_{out} = \frac{Q}{C} = \frac{1}{C} \int I dt \cong \frac{1}{C} \int \frac{V_{in}}{R} dt$$

$$V_{out} = \frac{1}{CR} \int V_{in} dt$$



RC differentiator

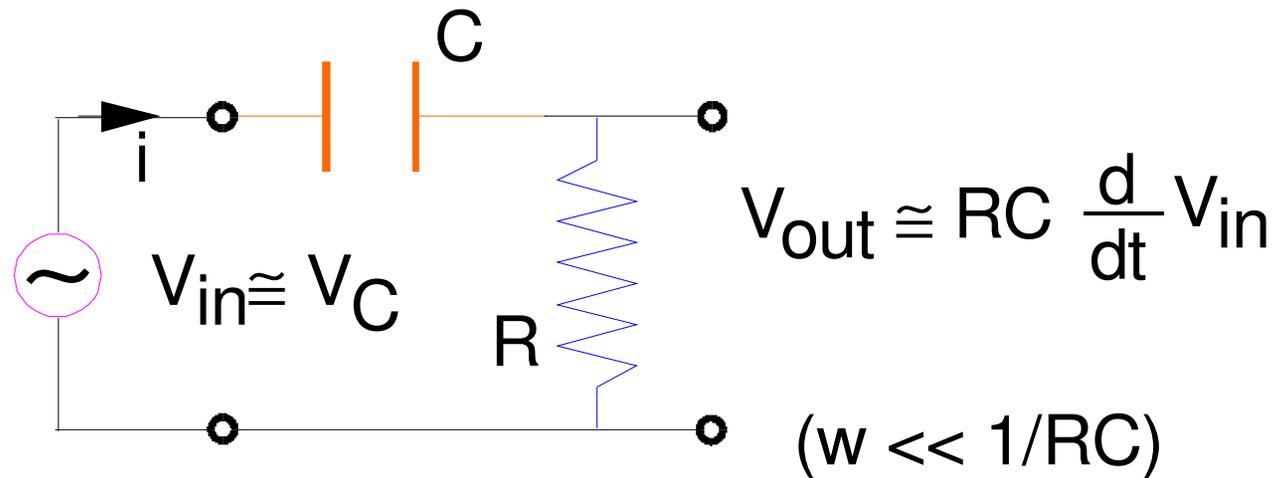


$$R \ll \frac{1}{\omega C} \Rightarrow V_{in} \cong \frac{I}{\omega C} = V_C$$

$$V_{out} = RI = R \frac{dQ}{dt} = R \frac{d}{dt} CV_c = RC \frac{dV_c}{dt}$$

$$V_{out} \cong RC \frac{d}{dt} V_{in}$$



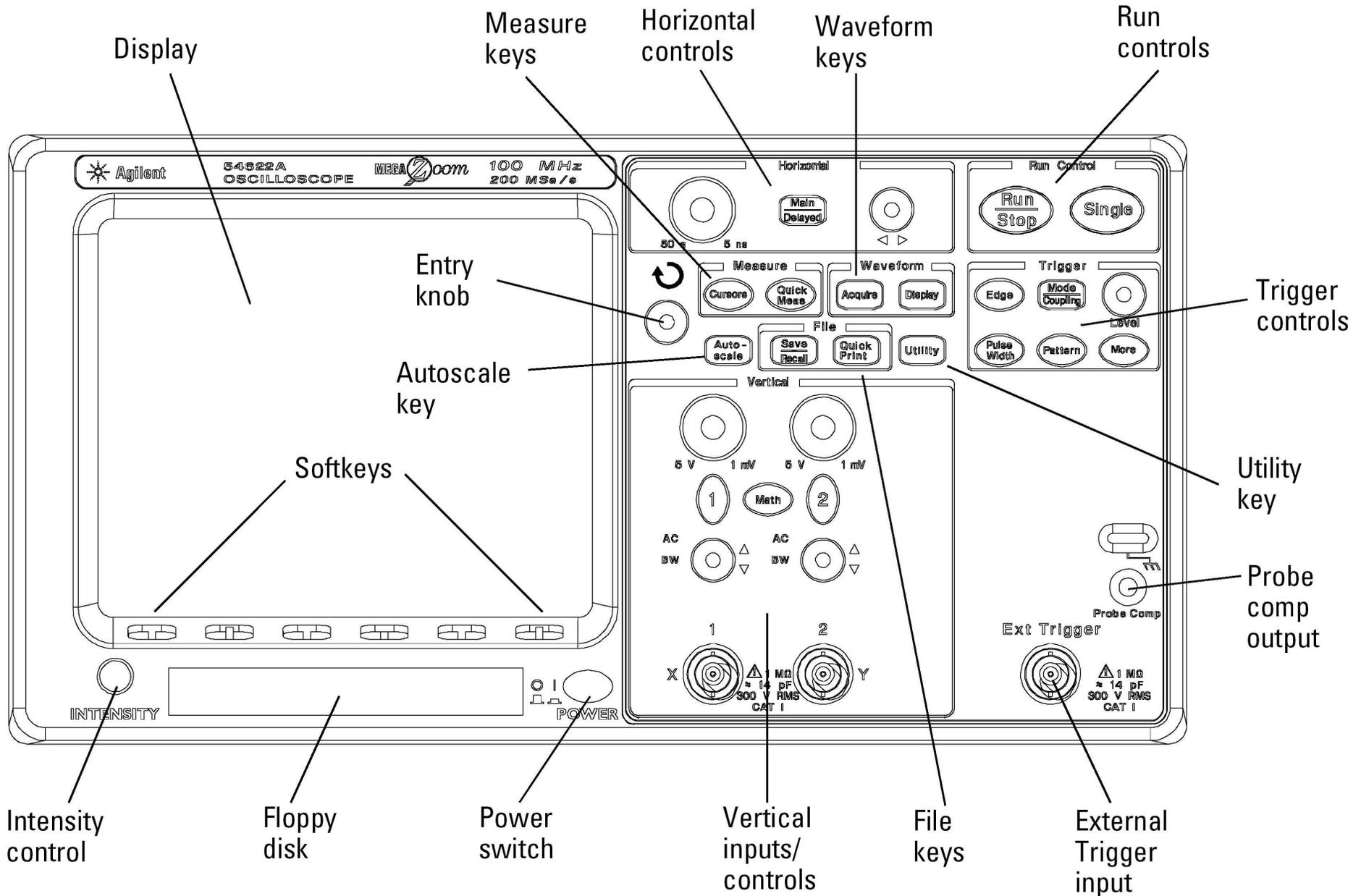303 – Physics for Engineers II - Laboratory Experimental procedure (1/10)



Experimental procedure (2/10)


1. Measuring probe compensation signal:

Probe compensation signal

Autoscale key

Display information and adjustment of scaling and position

Vertical sensitivity
ch 1 & 2: 2 V/div

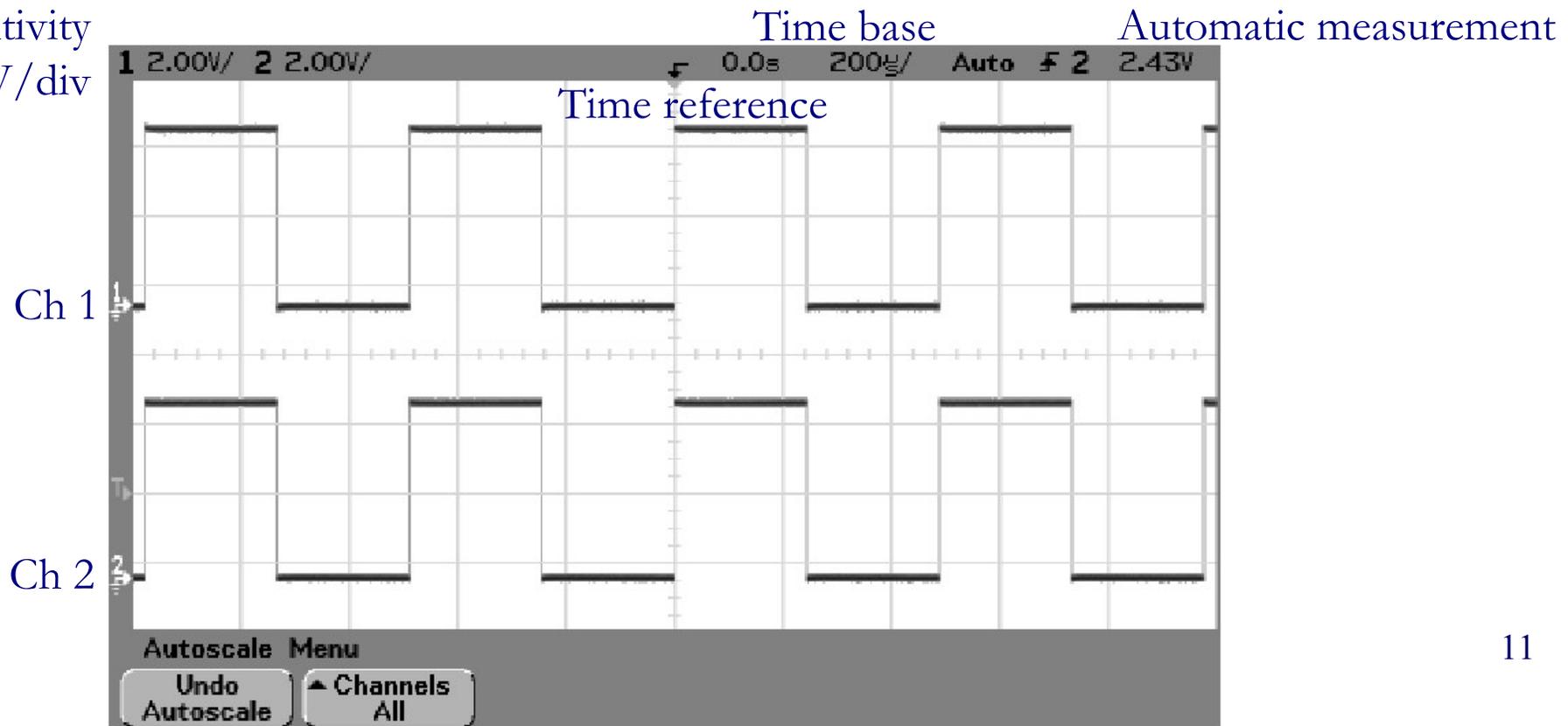


Experimental procedure (3/10)

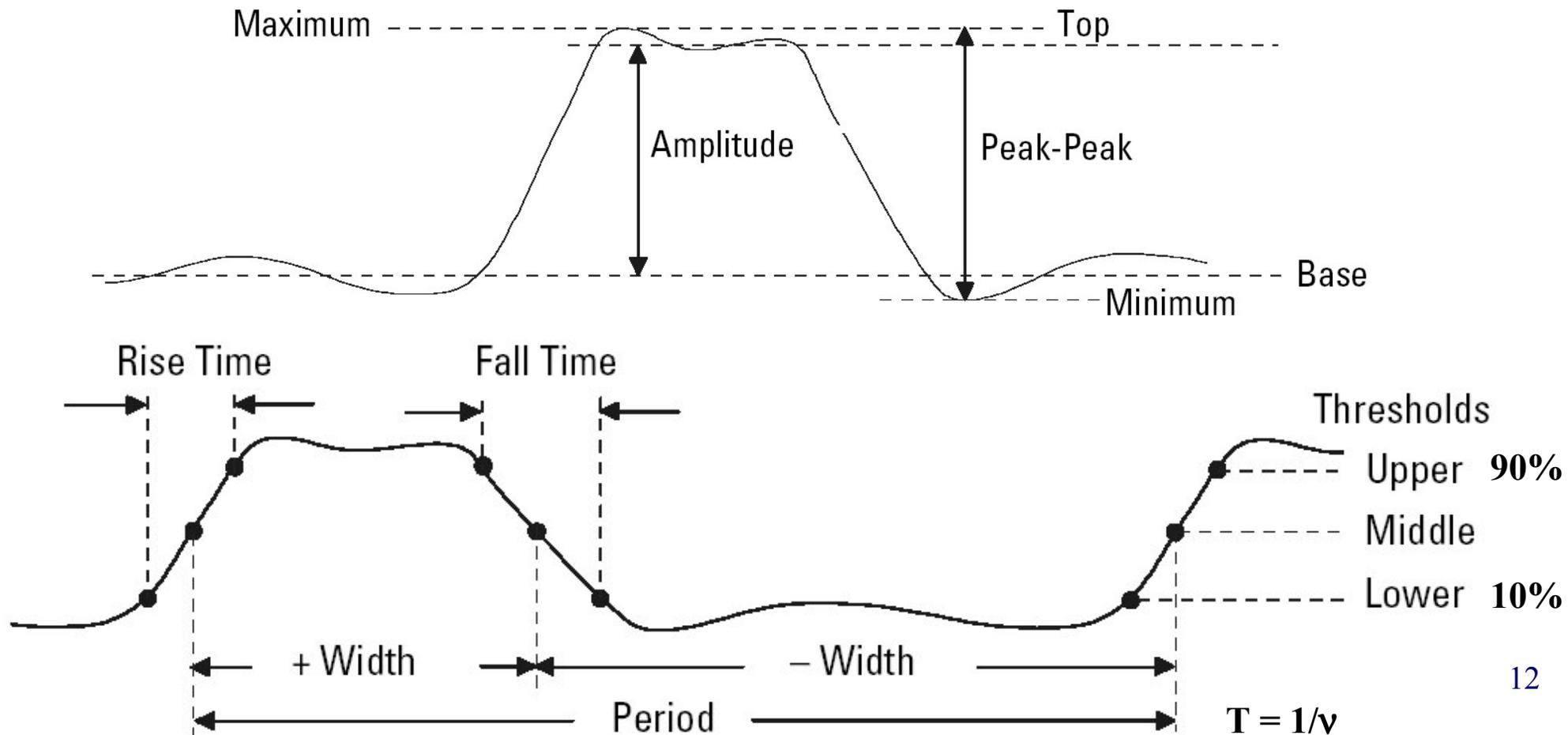1. Measuring probe compensation signal:



Checking probe attenuation factor

Automatic measurements of voltage and time: V_{pp} , V_{avg} (average), V_{rms} , ...



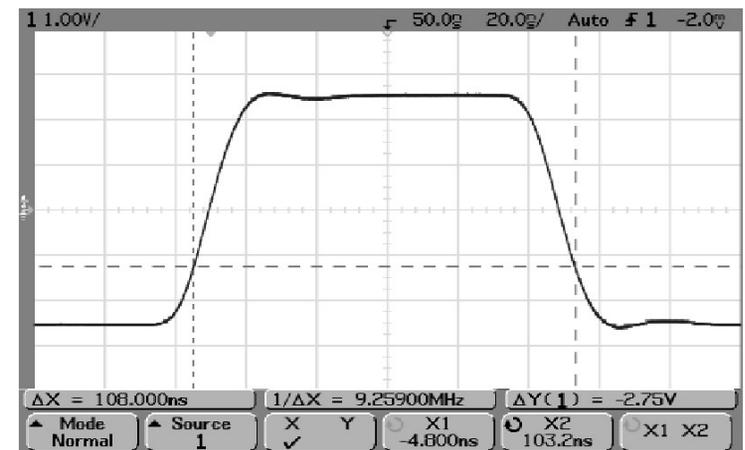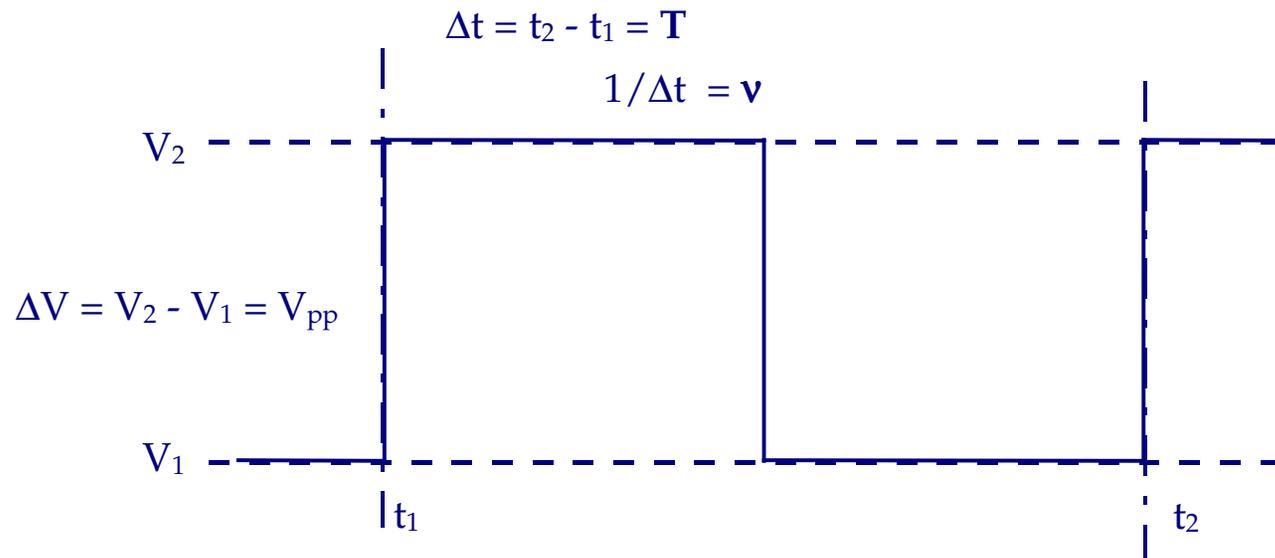1. Measuring probe compensation signal:

Voltage and time cursor measurement: V_{pp} , T and v




Experimental procedure (5/10)

1. Measuring probe compensation signal:

Main and delayed sweep

Trigger

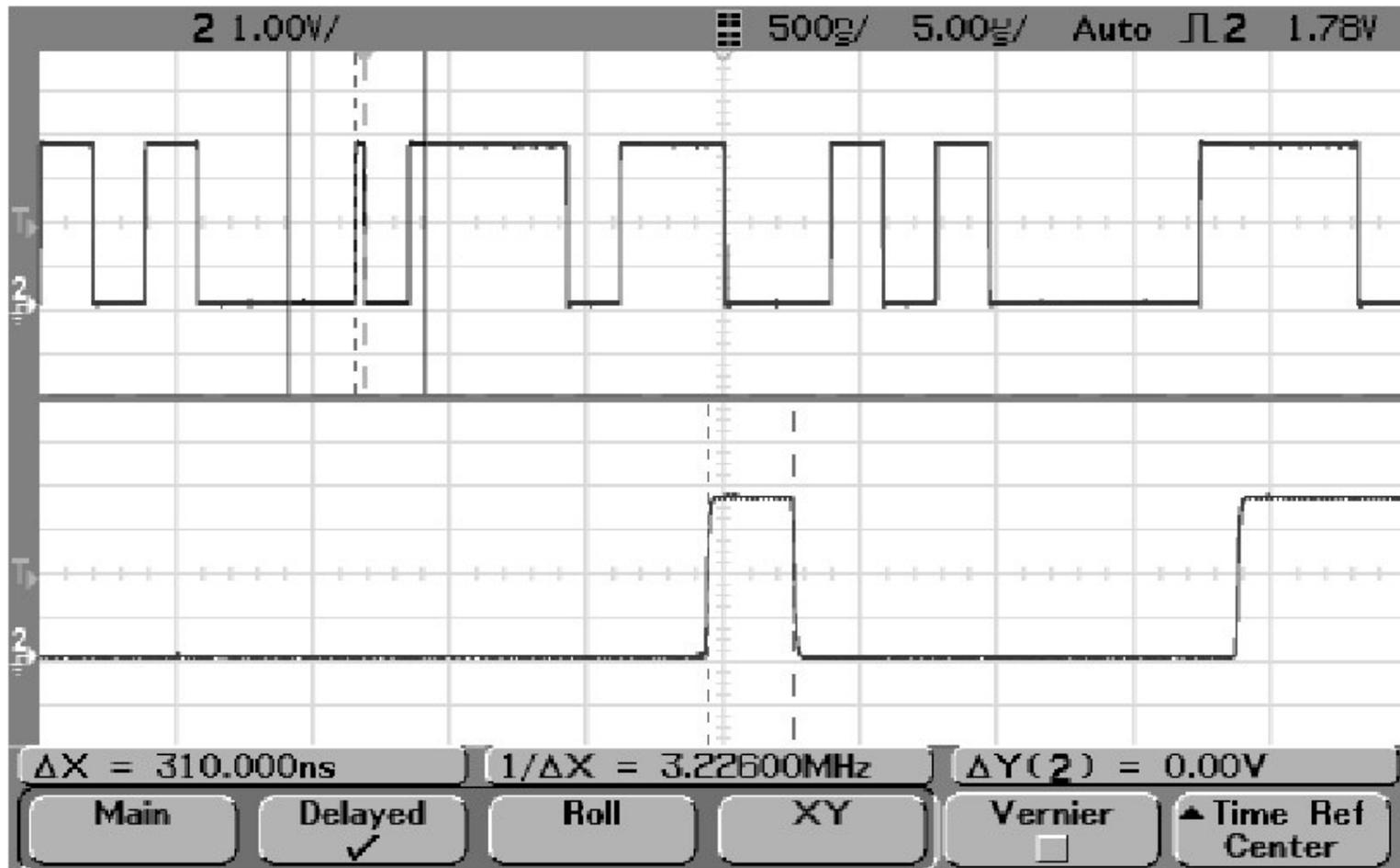

Experimental procedure (6/10)

1. **Measuring probe compensation signal.**
2. **Measuring ambient signals.**
3. **Measuring signals from function generator:**

Coaxial cable attenuation factor

7 kHz and 7 Hz signals

Adjust amplitude and offset


Experimental procedure (7/10)

4.1 Measuring transients: outputs 9 & 10, training signal board

9: Trigger: Single, mode Normal, \lrcorner , level 5.0 V. Time base: Left, 20 $\mu\text{s}/\text{div}$, 2V/div

10: as previous, but Trigger level 2V, sensitivity 1V/div

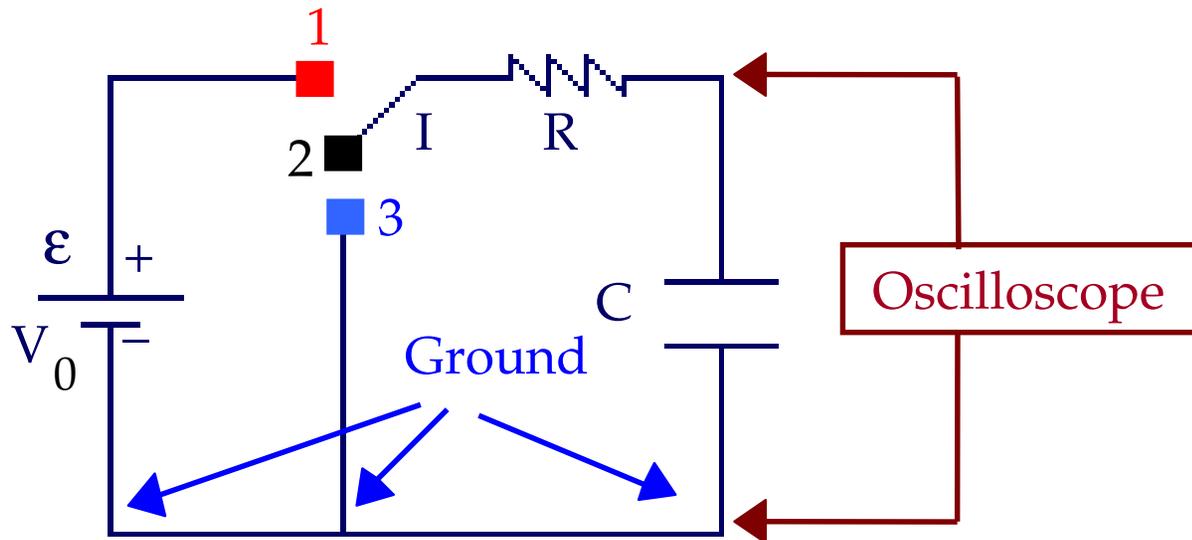4.2 Measuring transients: Discharging a capacitor




$R = 10 \text{ k}\Omega$, measure it!

$C = 1 \mu\text{F}$

Source 4 V

Trigger: Single, Level $< 4 \text{ V}$, Slope \lrcorner , 1 V/div, 5 ms/div, t Left

4.2 Discharging a capacitor

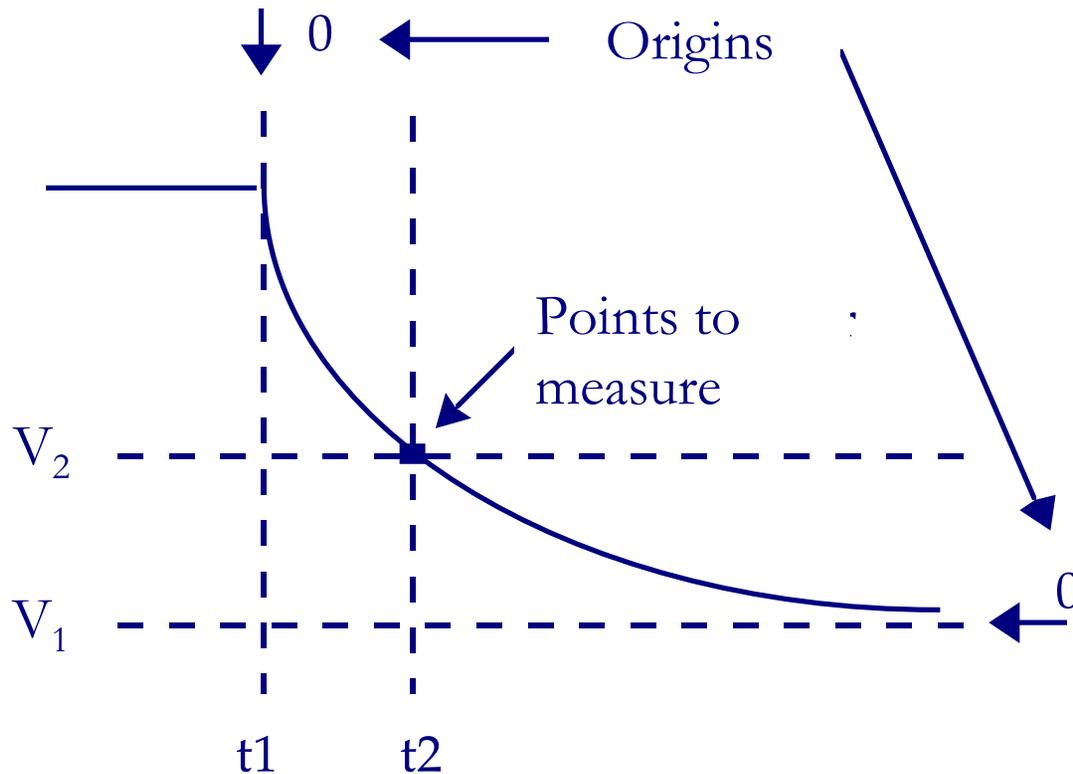

t (s)	V (V)	ln V

$$\ln V = -\frac{t}{RC} + \ln V_0$$

$$y = ax + b \quad a = \frac{-1}{RC}$$

Results: Calculation of τ , C i V_0 , and their uncertainty

Experimental procedure (9/10)

5.1 RC integrator



Circuit set-up: $C=1 \text{ nF}$ and $R=10 \text{ k}\Omega$.

Function generator: high frequency square wave ($\underline{v \approx 400 \text{ kHz}}$)

Channel 1, measuring input voltage.

Channel 2, measuring voltage across capacitor.

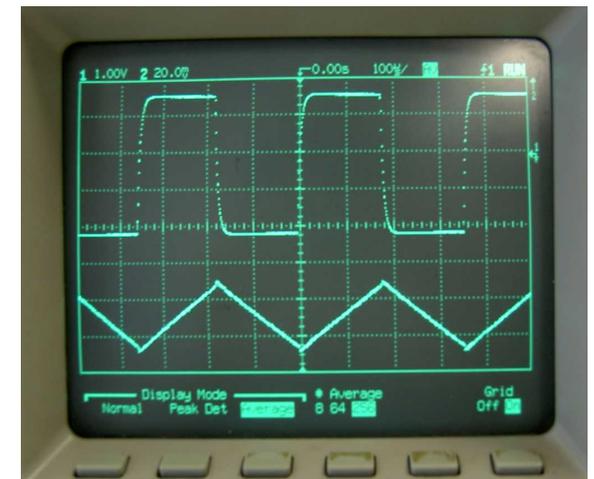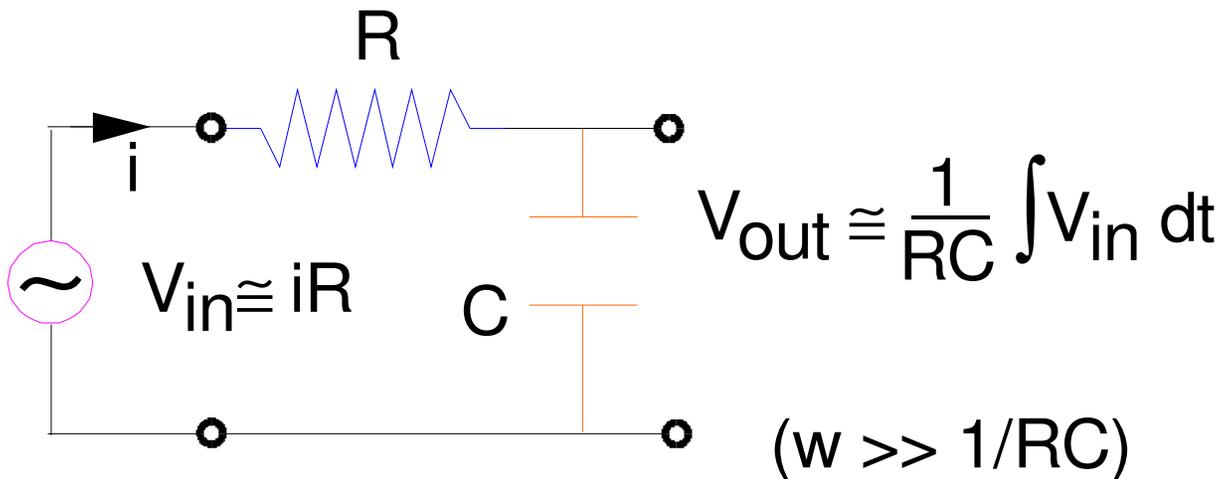Probe ground leads should be connected to the same point in the circuit



Experimental procedure (10/10)

5.2 RC differentiator



Circuit set-up: $C=470 \text{ nF}$ i $R= 10 \text{ k}\Omega$.

Function generator: low frequency triangle wave ($\nu \approx 100 \text{ Hz}$)

Channel 1, measuring input voltage.

Channel 2, measuring voltage across resistor.

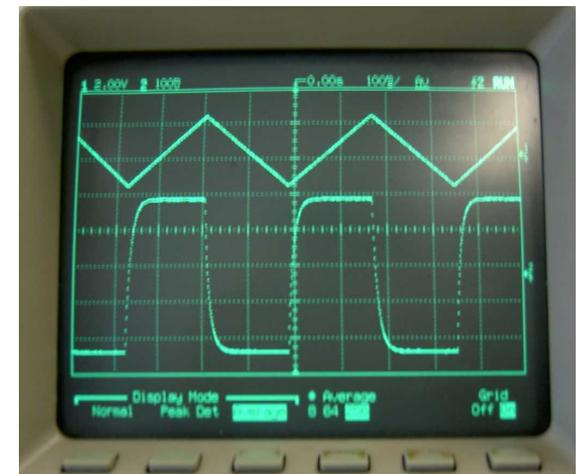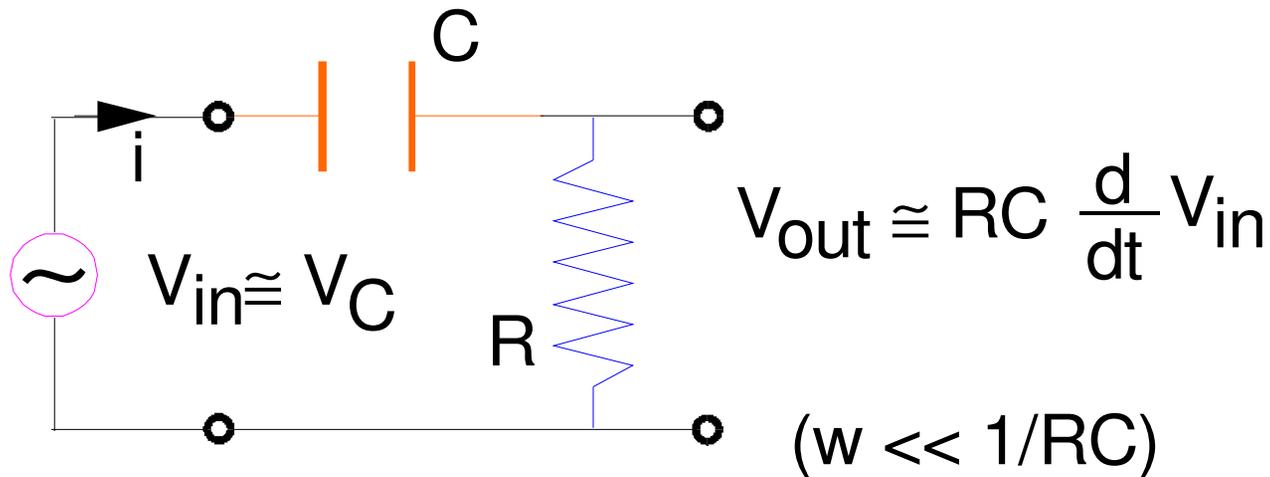Probe ground leads should be connected to the same point in the circuit



Questions

1.- What is the physical meaning of the time constant

$\tau = RC$ that appears in equation (9) in lab manual?

2.- Bearing in mind the input signal, justify the shape of the integral and derivative obtained in the oscilloscope from the RC circuit.