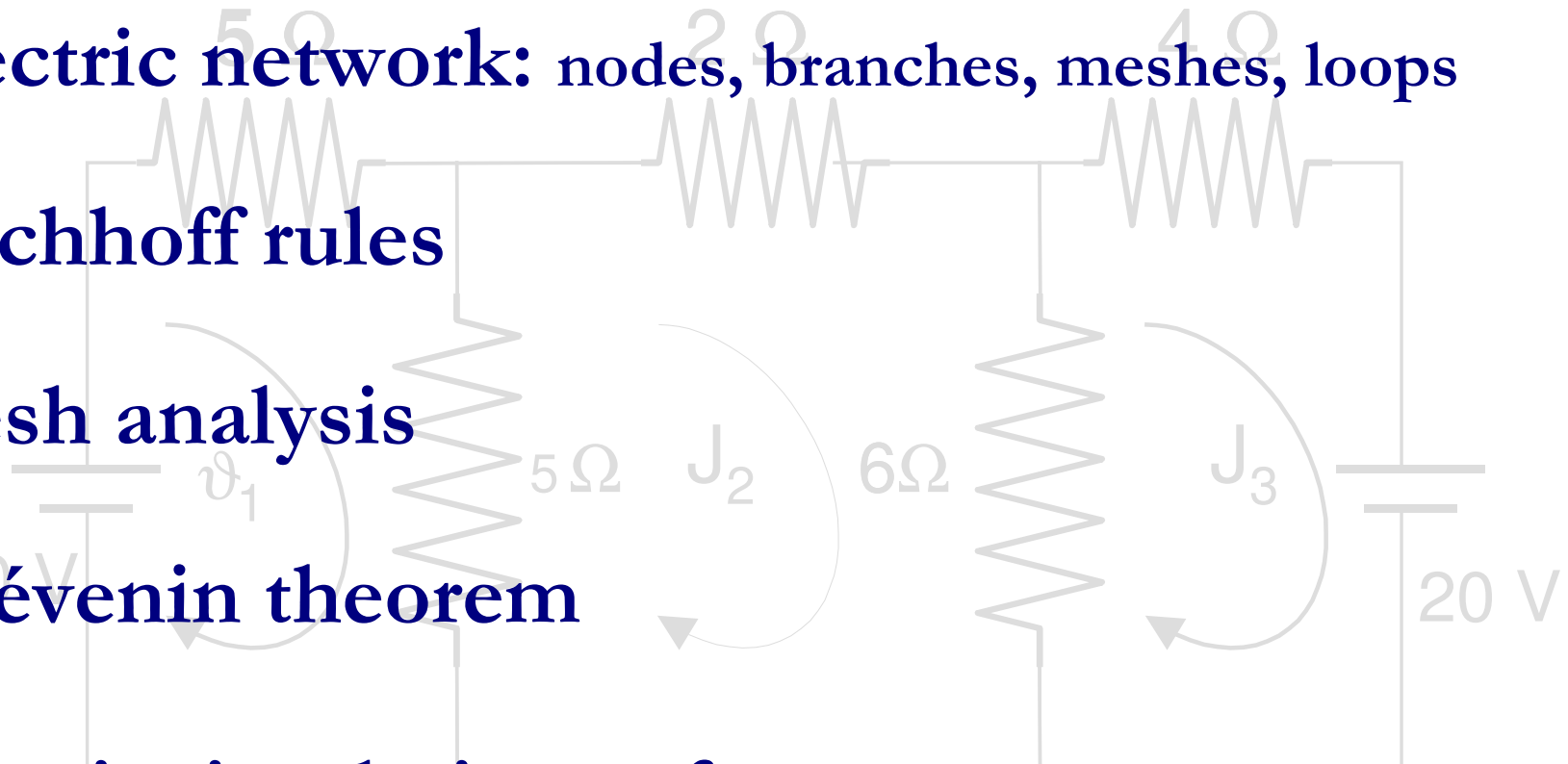




Experiment # 4: Simulation of electric circuits. Thévenin theorem

- **Electric network:** nodes, branches, meshes, loops
- **Kirchhoff rules**
- **Mesh analysis**
- **Thévenin theorem**
- **Circuit simulation software:** *Electronics Workbench*








Basic definitions:

Electrical network: A number of elements connected together forming a set of interrelated circuits.

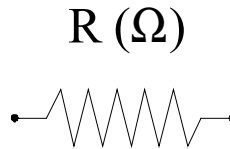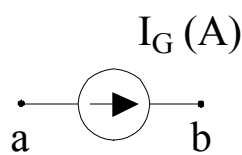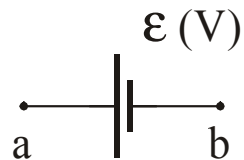Active (source of energy) and passive elements (resistors, etc.):




Node: Point where three or more circuit elements are joined together.

Branch: Conducting path between two nodes.

Loop: Any closed conducting path in the network.

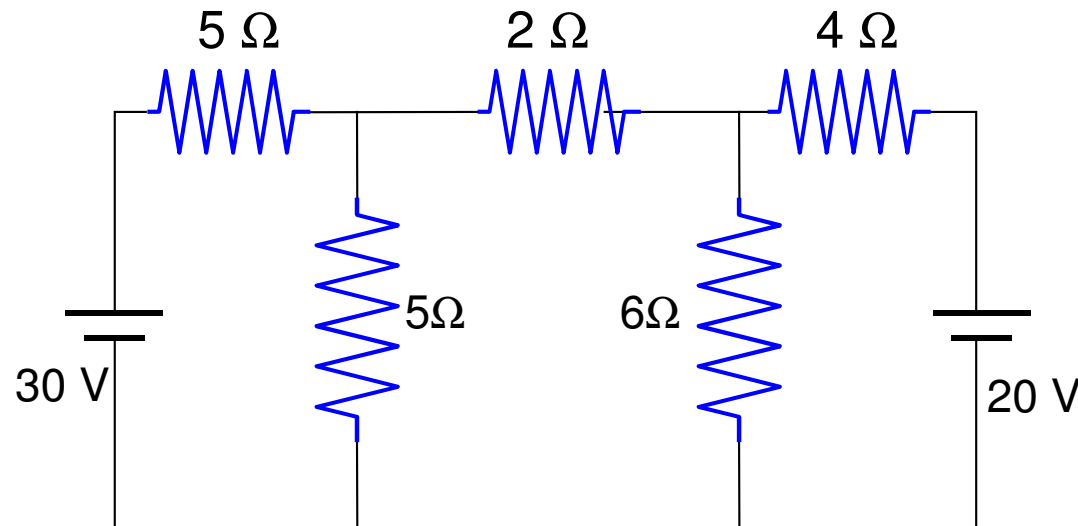Mesh: Loop of a circuit that does not contain any other loops within it.





Kirchhoff's Laws of electric circuits

Junction rule (based on charge conservation), also Kirchhoff's current law (KCL):

In any junction of the circuit,

$$\sum i_{entering} = \sum i_{leaving}$$

Loop rule (based on energy conservation), also Kirchhoff's voltage law (KVL):

Around any closed loop in a circuit,


$$\sum_k \pm i_k R_k = \sum_k \pm \varepsilon_k$$

Sign convention:

Across a resistor, voltage drop >0 in the direction of i

Through a battery, potential difference >0 from $+$ to $-$ terminal

Loop rule

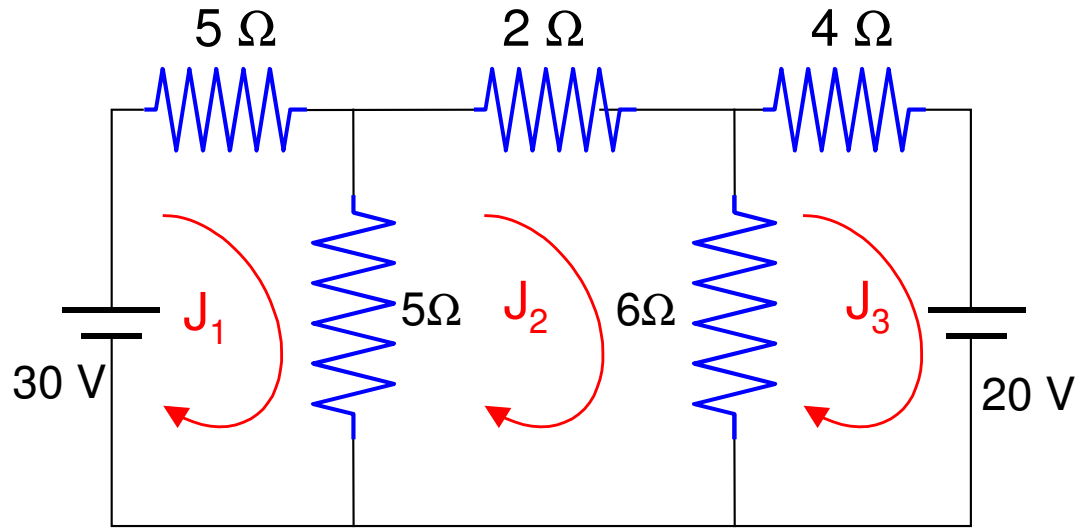

1. We choose a system of independent loops, including every branch in the circuit
2. We assign a number to each mesh, and choose an arbitrary current direction (same direction for every mesh, so opposite sign in shared branches)

3. We apply Kirkhhoff's loop rule, then we get n equations with n unknowns:

$$\sum_k (i_j - i_k) R_{jk} = \sum_k fem_{jk} \quad j=1,2,\dots$$



Loop rule

$$\begin{pmatrix} R_{11} & R_{12} & \dots & R_{1n} \\ R_{21} & R_{22} & \dots & R_{2n} \\ \dots & \dots & \dots & \dots \\ R_{n1} & R_{n2} & \dots & R_{nn} \end{pmatrix} \begin{pmatrix} J_1 \\ J_2 \\ \dots \\ J_n \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ \dots \\ V_n \end{pmatrix}$$

- R_{ii} sum of resistances in mesh i
- $R_{ij} = R_{ji}$ sum of resistances shared by meshes i and j , with opposite sign
- J_i current mesh i
- V_i sum of e.m.f. mesh i , with sign of exit pole


$$J_i = \frac{\begin{vmatrix} R_{11} & R_{12} & \dots & R_{1,i-1} & V_1 & R_{1,i+1} & \dots & R_{1n} \\ R_{21} & R_{22} & \dots & R_{2,i-1} & V_2 & R_{2,i+1} & \dots & R_{2n} \\ \dots & \dots & \dots & \dots & \dots & \dots & \dots & \dots \\ R_{n1} & R_{n2} & \dots & R_{n,i-1} & V_n & R_{n,i+1} & \dots & R_{nn} \end{vmatrix}}{\Delta_R}$$

$$\Delta_R \equiv \begin{vmatrix} R_{11} & R_{12} & \dots & R_{1n} \\ R_{21} & R_{22} & \dots & R_{2n} \\ \dots & \dots & \dots & \dots \\ R_{n1} & R_{n2} & \dots & R_{nn} \end{vmatrix}$$




Thévenin theorem

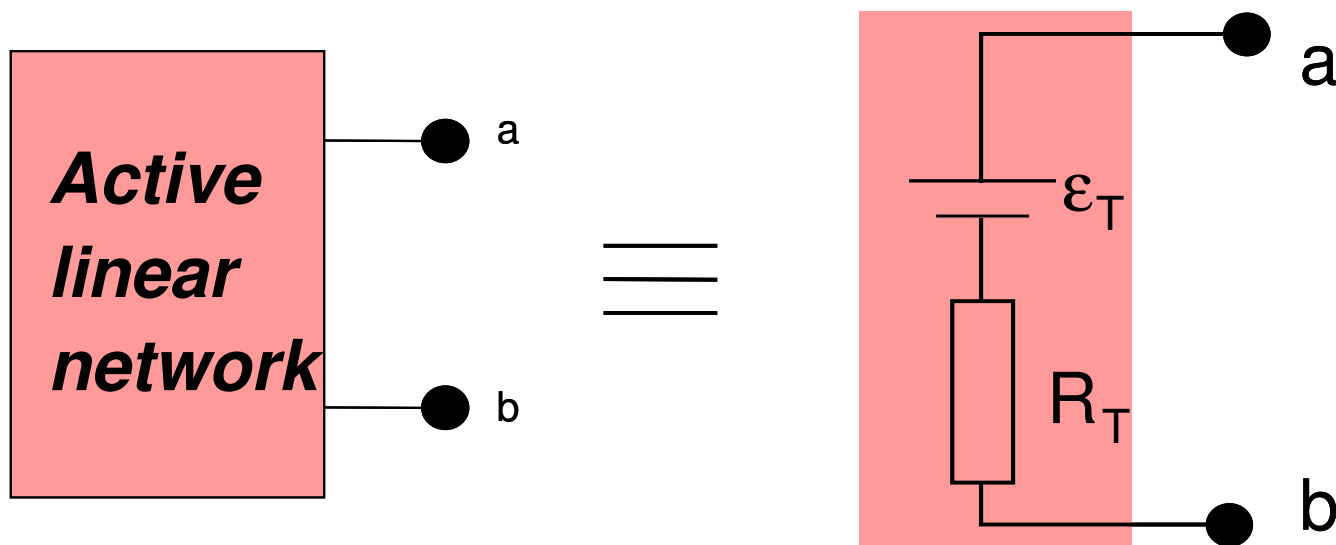Any two-terminal network of resistance elements and energy sources is equivalent to an ideal voltage source V_T in series with a resistor R_T , where V_T is the open-circuit voltage of the network, and R_T is the equivalent resistance when all energy sources are turned off (short-circuit for voltage sources, open-circuit for current sources).





1st step: theoretical circuit solution

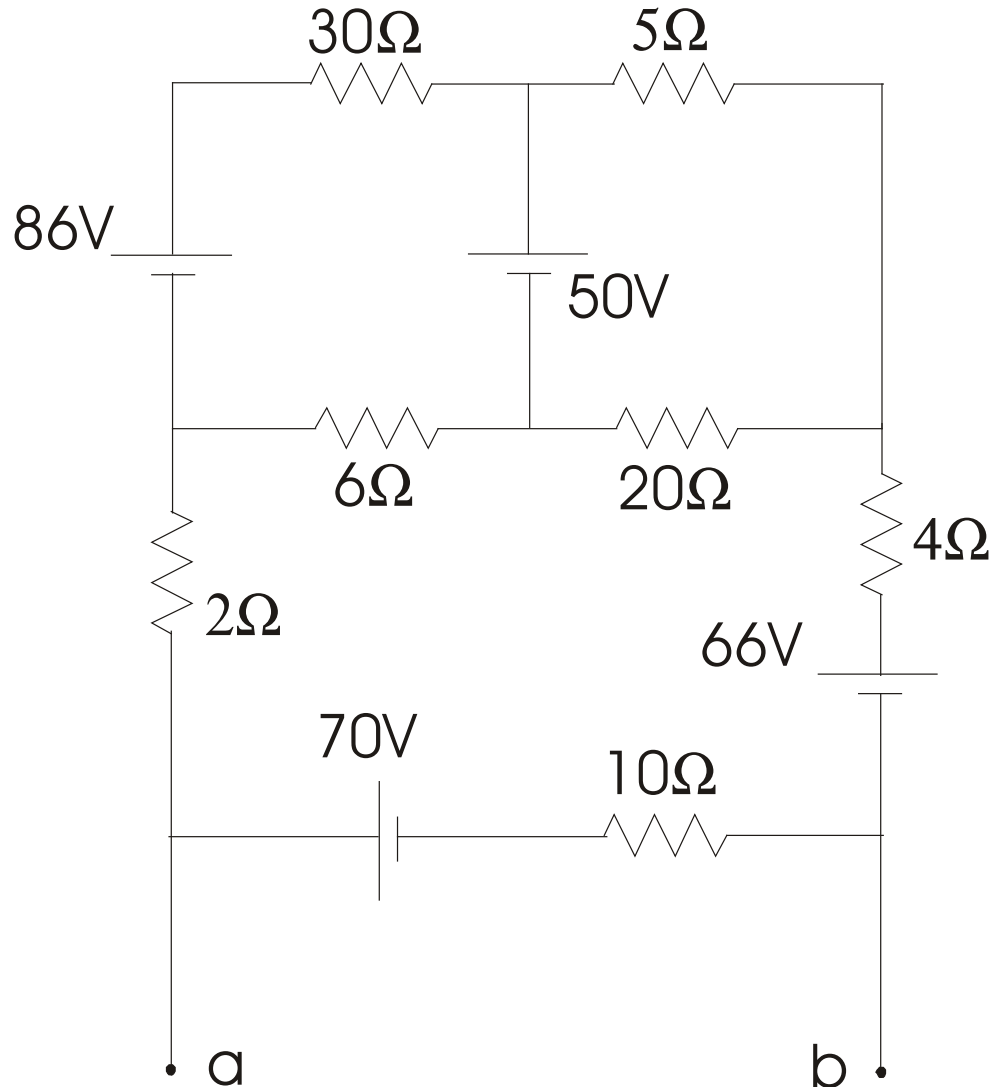


1. Find mesh currents
2. Determine V_{ab} , Thévenin voltage
3. Reduce voltage sources to zero by short-circuiting them and calculate equivalent resistance across points a and b, Thévenin resistance



303 – Physics for Engineers II - Laboratory


2nd part: Simulation with *EWB*

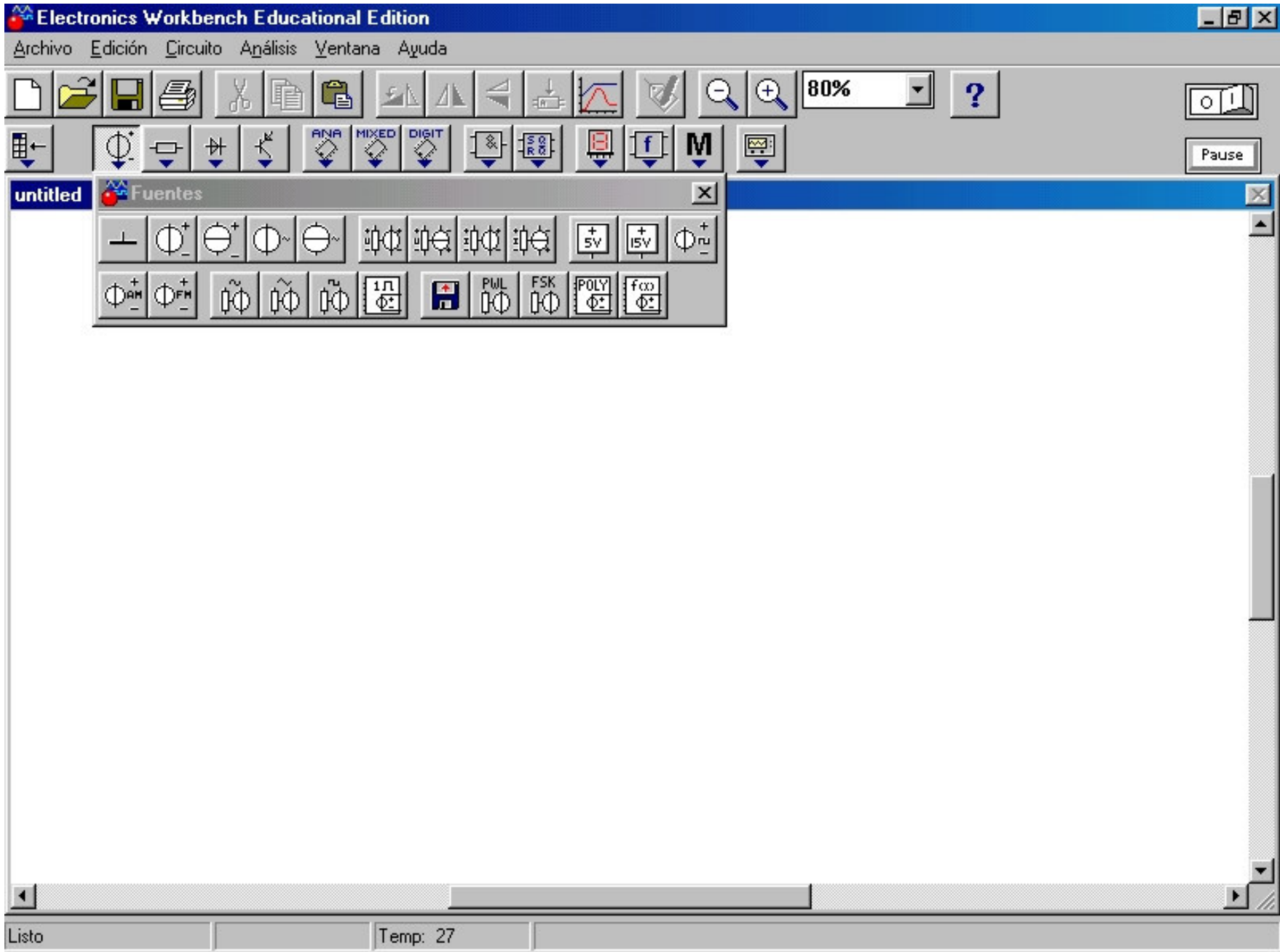



303 – Physics for Engineers II - Laboratory

2nd part: Simulation with *EWB*

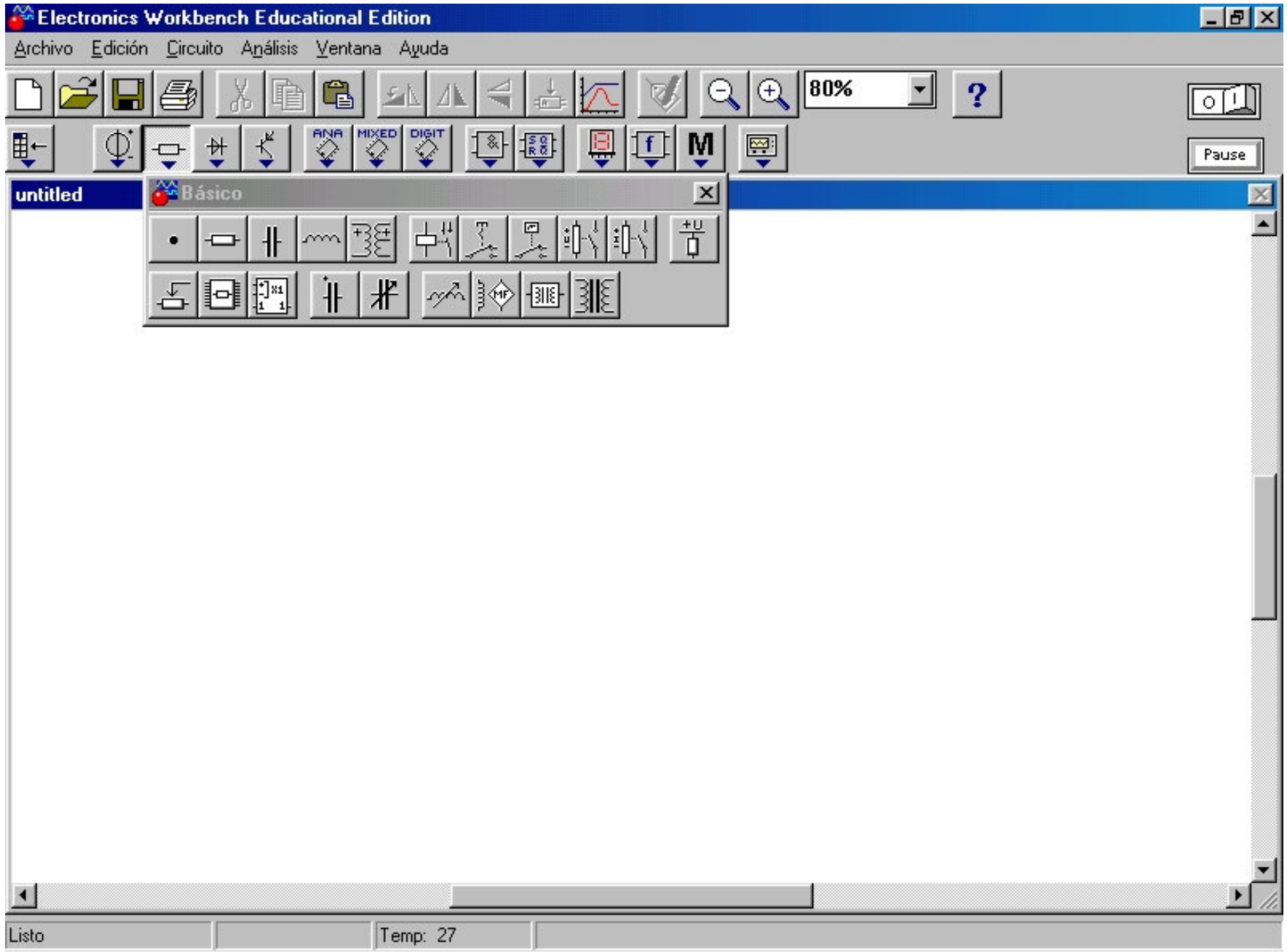



303 – Physics for Engineers II - Laboratory

2nd part: Simulation with *EWB*

The screenshot displays the Electronics Workbench Educational Edition software interface. The main window shows a circuit diagram with a 12V DC voltage source on the left, a 20 kΩ resistor in the top wire, and a 5 kΩ resistor connected in parallel to the bottom wire. A multimeter is connected in parallel across the 5 kΩ resistor. The multimeter's display shows a reading of 2.4000 V. The software interface includes a menu bar (Archivo, Edición, Circuito, Análisis, Ventana, Ayuda), a toolbar with various simulation and editing tools, and a status bar at the bottom showing 'Listo', '33.28 s', and 'Temp: 27'.



303 – Physics for Engineers II - Laboratory

2nd part: Simulation with *EWB*

303.ewb

Print the results you obtain!

Temp: 27